

CONTINUOUS INTERNAL EVALUATION - 3

Dept:EC	Sem / Div:IV A	Sub:Analog Circuits	S Code:18EC42
Date:30/08/2022	Time: 3:00-4:30 pm	Max Marks: 50	Elective:N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
PART A				
1 a	Explain the working of op-amp Non inverting amplifier. Derive the expression gain both exact and ideal analysis and get expressions for R_{if} , R_{of} and f_{of}	9	L2	CO4
b	For an inverting Schmitt Trigger circuit $R_1 = 15K\Omega$; $R_2 = 1K\Omega$ and $V_{in} = 10V_{p-pp}$ sine wave. The saturation voltages are $\pm 14V$ and $V_{ref} = 2 V$. i) Determine the threshold voltages V_{ut} and V_{lt} . ii) Find the value of Hysteresis voltage V_{hy} .	6	L2	CO4
c	What is an instrumentation amplifier? What are its applications? With a neat circuit diagram explain an instrumentation amplifier using a transducer bridge.	10	L3	CO4
OR				
2 a	Derive the expression for closed loop voltage gain, input and output resistance of inverting Amplifier. The opamp 741C is connected as an inverting amplifier with $R_1=1k\Omega$ and $R_F=4.7k\Omega$. Compute the closed loop parameters: A_F , R_{IF} , R_{OF} , f_F . Given $A=400000$, $R_i=33M\Omega$ and $R_O=60\Omega$; supply voltages are $\pm 13V$; Max output voltage swing = $\pm 13V$, Unity gain bandwidth = $0.6MHz$.	10	L2	CO4
b	Explain the operation of 4-bit R-2R DAC with neat circuit. For the R-2R DAC, with $R=10k\Omega$ and $R_F=20k\Omega$ and $V_{REF}=5V$, determine the output voltage when the inputs $b_0=b_1=5V$ and	9	L3	CO4

	b2=b3=0V			
c	Explain the working of a Successive Approximation type of ADC.	6	L2	CO4
PART B				
3 a	Derive an Expression for the output of a inverting Summing amplifier with three inputs and averaging amplifier	10	L2	CO4
b	Explain the operation of a monostable multivibrator with relevant diagrams and waveforms.	10	L2	CO4
c	Write the difference between Inverting and Non Inverting amplifier.	5	L2	CO4
OR				
4 a	Explain the basic comparator circuit using an opamp. How can this circuit be used in an application as a zero crossing detector?	10	L2	CO4
b	Design an Astable Multivibrator using 555 timer having output frequency of 10KHz with a dutyCycle of 25%.	6	L3	CO4
c	Explain the working of a second order high pass Butterworth filter with a neat circuit diagram and frequency response. Write the relevant design equations.	9	L2	CO4

Nisha

Prepared by: Nisha G R

G. hat

HOD